

Semester-II (FYUGP)

Paper: Electricity and Magnetism


Paper Code: PHY0200104

Unit-V (Network Theorems)


BY

Dr. S. Zamal

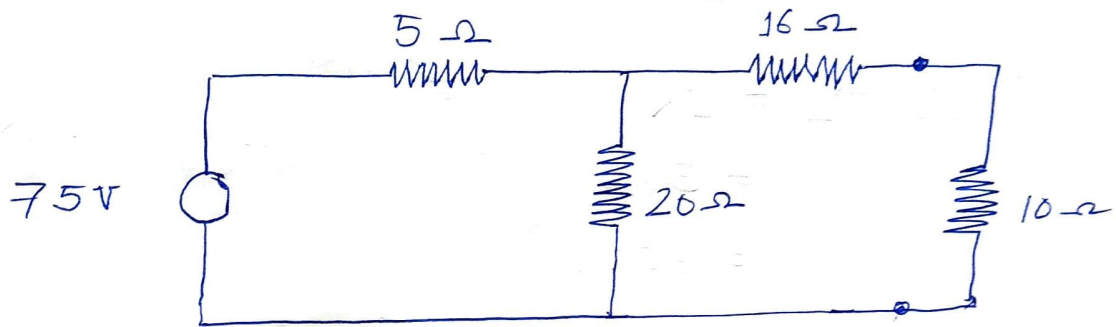
Ex: Transform the following circuit into Thevenin's equivalent circuit, and hence find the value of (a) Thevenin's equivalent ~~in~~ impedance, (b) Thevenin's equivalent voltage source, and (c) load current and power in the $10\ \Omega$ resistor. [TDC, Sem-V, GU-2016]



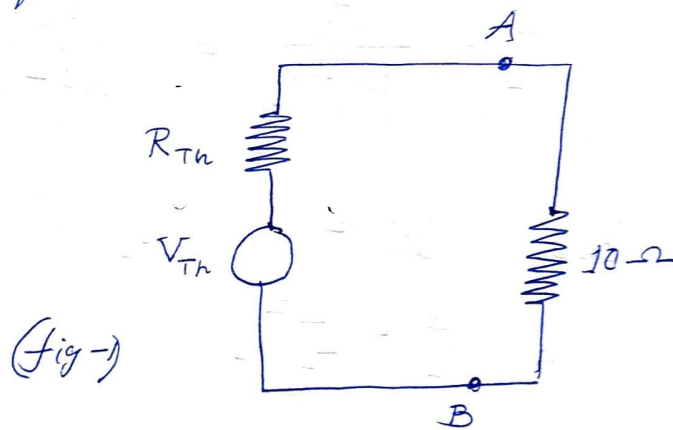Solution: Thevenin's equivalent circuit is shown in fig-1.



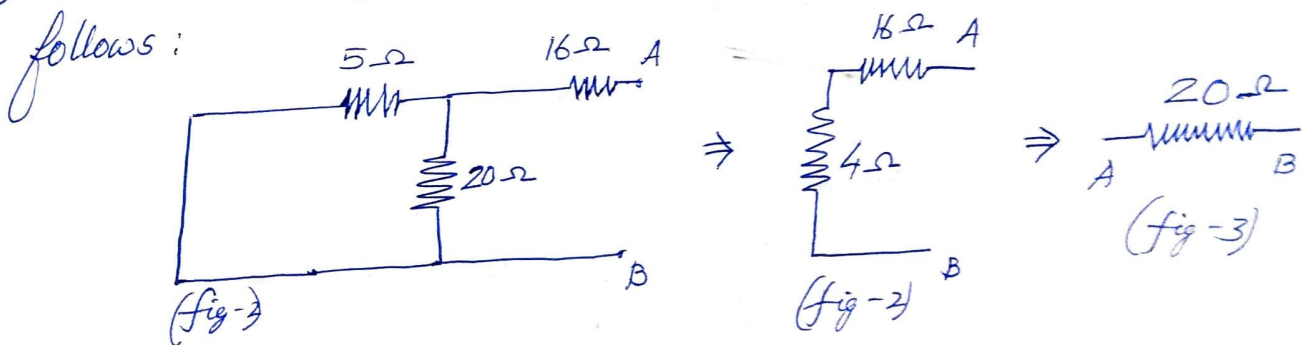(a) Thevenin's equivalent impedance R_{Th} is calculated as follows:



Thus $R_{Th} = 20\ \Omega$

Ex: An AC source of emf 40V delivers a maximum power of 10W to an external load resistance. What is the internal resistance of the source? How much current will be drawn from the source if the output terminals are short-circuited?

Solution: The networks contain only resistances. So

$$P_{\max} = \frac{E_{\text{rms}}^2}{4R_0}$$

$$\Rightarrow R_0 = \frac{E_{\text{rms}}^2}{4P_{\max}}$$

$$= \frac{40 \times 40}{4 \times 10}$$

$$= 40 \Omega.$$

For max power


$$P = \frac{E_{\text{rms}}^2 R_L}{(R_0 + R_L)^2 + (X_0 + X_L)^2}$$

Here $X_0 = X_L = 0$

$$\therefore P = \frac{E_{\text{rms}}^2 R_L}{(R_0 + R_L)^2} I$$

But $R_L = R_0$
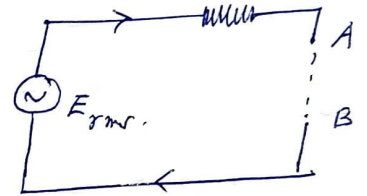
$$\therefore P_{\max} = \frac{E_{\text{rms}}^2}{4R_0^2}$$




The short circuit current will be

$$I = \frac{E_{\text{rms}}}{R_0}$$

$$= \frac{40}{40}$$


$$= \underline{\underline{1 \text{ A}}}$$

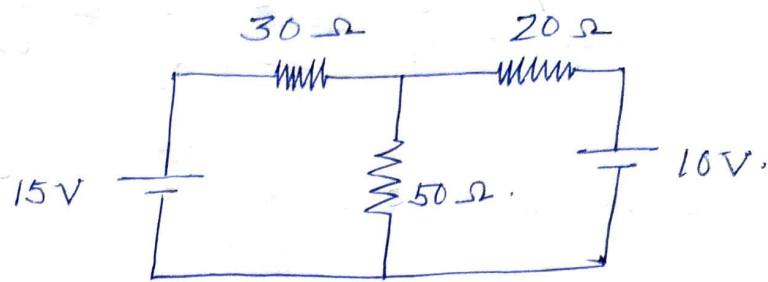Ex.: Apply superposition principle to determine the currents flowing through each branch of the network.




Verify the result using Kirchhoff's laws.

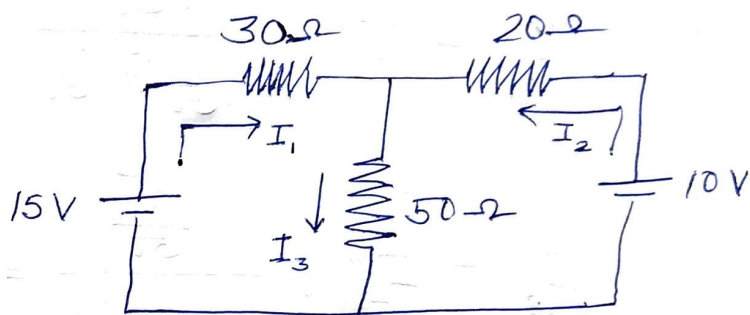
Solution: Let I_1 , I_2 and I_3 be the currents through the $30\ \Omega$, $20\ \Omega$ and the $50\ \Omega$ resistors respectively (fig-1).



(fig-1)

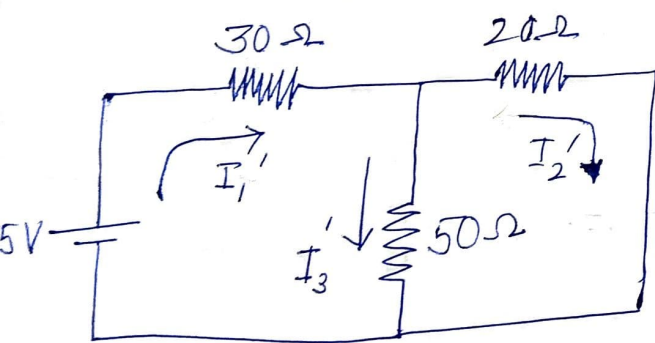

(fig-2)

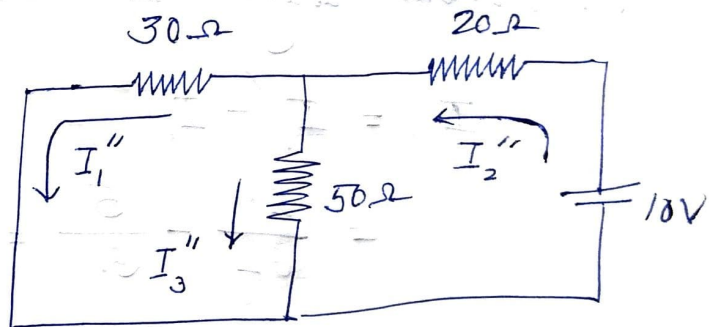

(fig-3)

In fig-2, the 10V source is removed. The currents are

$$I_1' = \frac{15}{30 + \frac{20 \times 50}{20 + 50}} = \frac{15}{30 + \frac{100}{7}} = \frac{105}{310} = \frac{21}{62} \text{ A.}$$

Using current division rule we get

$$I_2' = I_1' \frac{\frac{1}{30}}{\frac{1}{30} + \frac{1}{20}} = \frac{321}{62} \times \frac{1/20}{1/30 + 1/20} = \frac{21^3 \cdot 5}{62 \times 10} \text{ A} = \frac{15}{62} \text{ A}$$

$$I_3' = I_1' \times \frac{\frac{1}{50}}{\frac{1}{50} + \frac{1}{20}} = \frac{21}{62} \times \frac{1/50}{7/100} = \frac{3}{31} \text{ A.}$$

Now the 15 V source is removed (fig-3). We have

$$I_2'' = \frac{10}{20 + \frac{30 \times 50}{30 + 50}} = \frac{10}{20 + \frac{1500}{84}} = \frac{10 \times 4}{\frac{155}{31}} = \frac{8}{31} \text{ A.}$$

Current division rule gives

$$I_1'' = I_2'' \times \frac{1/30}{1/30 + 1/50} = \frac{8}{31} \times \frac{1/30}{8/150} = \frac{5}{31} \text{ A.}$$

$$I_3'' = I_2'' \times \frac{1/50}{1/50 + 1/30} = \frac{8}{31} \times \frac{1/50}{8/150} = \frac{3}{31} \text{ A.}$$

∴ Current through the 30 Ω resistor is

$$I_1 = I_1' - I_1'' = \frac{21}{62} - \frac{5}{31} = \frac{11}{62} \text{ A.}$$

$$I_2 = I_2' - I_2'' = \frac{15}{62} - \frac{8}{31} = \frac{15 - 16}{62} = -\frac{1}{62} \text{ A.}$$

i.e. $I_2 = \frac{1}{62} \text{ A}$ in the anticlockwise direction.

$$I_3 = I_3' + I_3''$$


$$= \frac{3}{31} + \frac{3}{31} = \frac{6}{31} \text{ A}$$

Verification by Kirchoff's laws.

Current distribution

in the three branches using KCL is shown

in fig-4.

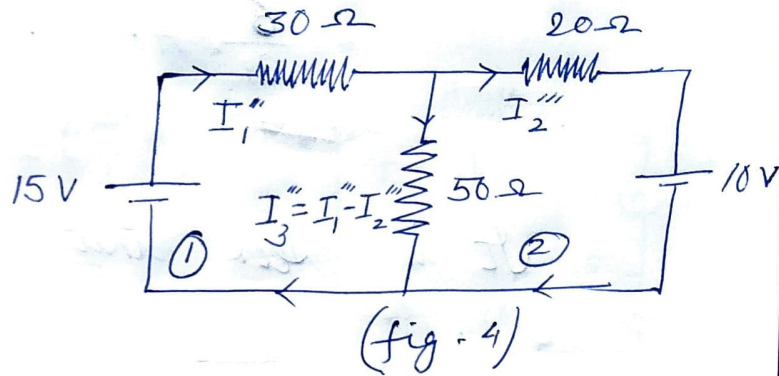

Using KVL to mesh ① we get

$$-30I_1'' - 50(I_1'' - I_2'') + 15 = 0.$$

$$\Rightarrow 6I_1'' + 10(I_1'' - I_2'') = 3$$

$$\Rightarrow 16I_1'' - 10I_2'' = 3 \rightarrow (1)$$

Using KVL to mesh ② we get.

$$-20I_2'' + 50(I_1'' - I_2'') - 10 = 0.$$

$$\Rightarrow 5I_1'' - 7I_2'' = 1 \rightarrow (2)$$

Using Cramer's rule we get

$$I_1'' = \frac{\begin{vmatrix} 3 & -10 \\ 1 & -7 \end{vmatrix}}{\begin{vmatrix} 16 & -10 \\ 5 & -7 \end{vmatrix}} = \frac{-21 + 10}{-112 + 50} = \frac{-11}{-62} = \frac{11}{62} \text{ A.}$$

$$I_2'' = \frac{\begin{vmatrix} 16 & -3 \\ 5 & -1 \end{vmatrix}}{\begin{vmatrix} 16 & -10 \\ 5 & -7 \end{vmatrix}} = \frac{-16 - 15}{-62} = -\frac{1}{62} \text{ A.}$$

ie $I_2'' = \frac{1}{62} A$ in anticlockwise direction

$$\text{And } I_3''' = I_1'' - I_2'''$$

$$= \frac{11}{62} - \left(-\frac{1}{62}\right)$$

$$= \frac{106}{62}$$

$$= \frac{6}{31} A$$

It is seen that $I_1''' = I_1$

$$I_2''' = I_2$$

and $I_3''' = I_3$

verified.